

TITLE:Mobile cellphone charger

DESCRIPTION:

Basically, the charger is a current-limited voltage source. Generally, cellphone battery packs require 3.6-6V DC and 180-200mA current for charging. These usually contain three NiCd cells, each having 1.2V rating. Current of 100mA is sufficient for charging the cellphone battery at a slow rate. A 12V battery containing eight pen cells gives sufficient current (1.8A) to charge the battery connected across the output terminals. The circuit also monitors the voltage level of the battery. It automatically cuts off the charging process when its output terminal voltage increases above the predetermined voltage level.

Timer IC NE555 is used to charge and monitor the voltage level in the battery. Control voltage pin 5 of IC1 is provided with a reference voltage of 5.6V by zener diode ZD1. Threshold pin 6 is supplied with a voltage set by VR1 and trigger pin 2 is supplied with a voltage set by VR2.

When the discharged cellphone battery is connected to the circuit, the voltage given to trigger pin 2 of IC1 is below $1/3V_{cc}$ and hence the flip-flop in the IC is switched on to take output pin 3 high. When the battery is fully charged, the output terminal voltage increases the voltage at pin 2 of IC1 above the trigger point threshold. This switches off the flip-flop and the output goes low to terminate the charging process. Threshold pin 6 of IC1 is referenced at $2/3V_{cc}$ set by VR1. Transistor T1 is used to enhance the charging current. Value of R3 is critical in providing the required current for charging. With the given value of 39-ohm the charging current is around 180 mA.

The circuit can be constructed on a small general-purpose PCB. For calibration of cut-off voltage level, use a variable DC power source. Connect the output terminals of the circuit to the variable power supply set at 7V. Adjust VR1 in the middle position and slowly adjust VR2 until LED1 goes off, indicating low output. LED1 should turn on when the voltage of the variable power supply reduces below 5V. Enclose the circuit in a small plastic case and use suitable connector for connecting to the cellphone battery.

The main part of the circuit mobile cellphone charger is timer IC NE555, used to

charge and monitor the voltage level. IC₁ get control voltage to pin 5 by zener diode ZD₁. Threshold pin 6 and trigger pin 2 is supplied with a voltage set by

VR₁ and VR₂ respectively. The trigger pin 2 of IC₁ is below $\frac{1}{3}V_{CC}$ when

discharge battery is connected to the circuit as a result flip-flop of IC₁ is switched

on to take output pin 3 high. The process is reversed when battery is fully charged

of charged battery is connected. Here transistor T₁ used to enhance the charging current from output pin 3 of IC₁. Adjust potentiometer VR₁ and VR₂ as per require

LED status for different charging conditions

Load across the output	Output frequency (at pin 3)	LED ₁
Charging battery	4.5 Hz	On
Fully charged battery	0	Off

CIRCUIT DIAGRAM

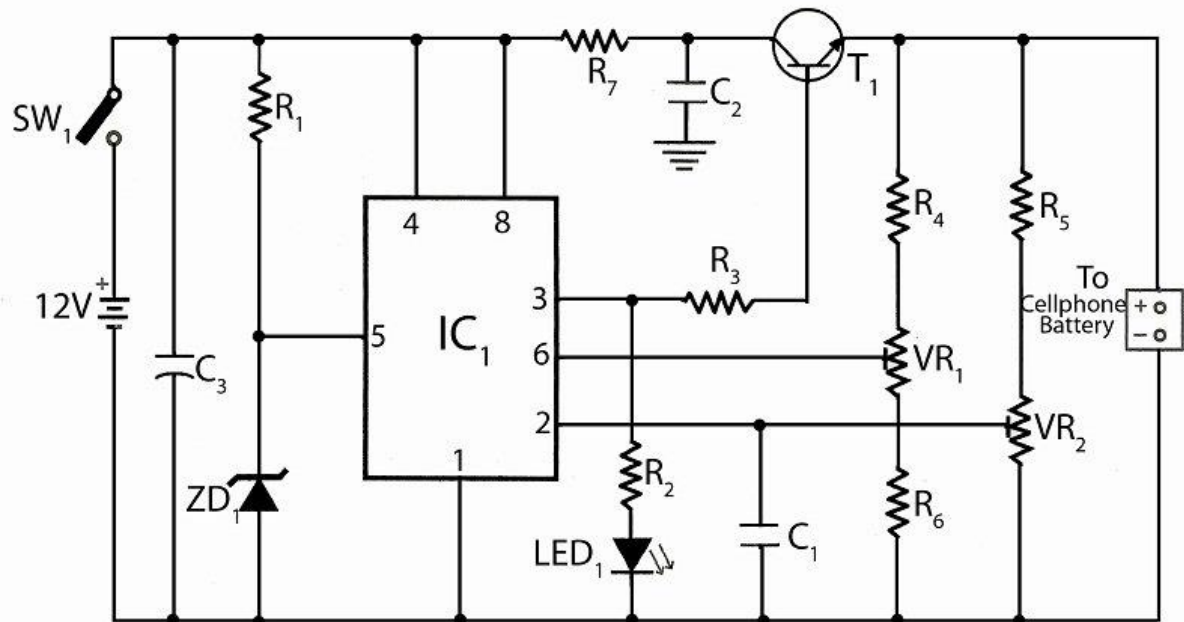


Figure 1: Mobile Cellphone Charger

PARTS LIST

Resistors (all 1/4-watt, $\pm 5\%$ Carbon)

$R_1 = 390 \Omega$, $R_2 = 680 \Omega$, $R_3 = 39 \Omega/1W$, $R_4 = 27 K\Omega$, $R_5 = 47 K\Omega$, $R_6 = 3.3 K\Omega$, $R_7 = 100 \Omega/1W$, $VR_1, VR_2 = 20 K\Omega$

Capacitors

$C_1 = 0.001 \mu F$ (ceramic disc), $C_2 = 0.01 \mu F$ (ceramic disc), $C_3 = 4.7 \mu F/25V$ (Electrolytic)

Semiconductors

$IC_1 = NE555$ timer IC, $T_1 = SL100$ or any Medium power general purpose NPN transistor like: 2N4922 , 2N4921, 2N4238, FCX1053A

$ZD_1 = 5.6 \text{ V}/1\text{W}, \text{LED}_1$

Miscellaneous

$SW_1 = \text{On/off switch}, 1.5\text{V} \times 8 \text{ AA cells}, \text{Mobile connector}$

TEAM MEMBERS:

K KARTHIKEYA ,411530

K CHAKRADHAR ,411531